

Settimana: 10

Argomenti:


Materia: Fisica

Classe: 5F

Data: 17/11/25

Pag 268 n 64

(a)

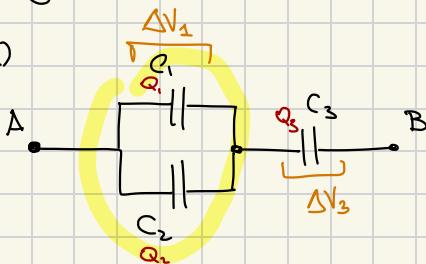

$$C_1 = 350 \text{ pF} = 350 \cdot 10^{-12} \text{ F}$$

$$C_2 = 520 \cdot 10^{-12} \text{ F}$$


$$C_3 = 230 \cdot 10^{-12} \text{ F}$$

$$\Delta V_{AB} = 350 \text{ kV} = 350 \cdot 10^3 \text{ V}$$

1)  $C_{eq} = ?$

2)  $Q_1, Q_2, Q_3, \Delta V_1, \Delta V_2, \Delta V_3$


(b)

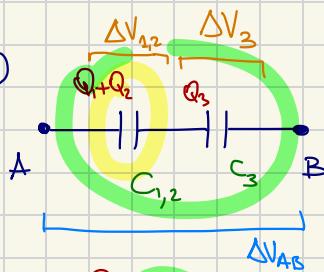

$$C_{1,2} = C_1 + C_2 \quad \text{per le formule viste in classe}$$

$$Q_3 = Q_1 + Q_2 \quad \text{perché le cariche si dispongono nel filo}$$

(c)

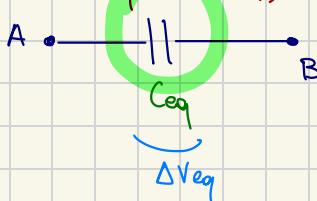

$$\frac{1}{C_{eq}} = \frac{1}{C_{1,2}} + \frac{1}{C_3} \quad \text{Per le formule in classe}$$

Ho tutto:  $C_{eq} = \frac{C_{1,2} \cdot C_3}{C_{1,2} + C_3} \quad \text{=} \quad \frac{(C_1 + C_2) C_3}{C_1 + C_2 + C_3} \quad \approx 182 \text{ pF}$

(2) Torniamo indietro: (c)  $C_{eq} = \frac{Q_{eq}}{\Delta V_{eq}}$

$$\rightsquigarrow Q_{eq} = Q_3 = C_{eq} \frac{\Delta V_{eq}}{\Delta V_{AB}} = 243 \text{ nC}$$

$$(b) C_3 = \frac{Q_3}{\Delta V_3} \rightarrow \Delta V_3 = \frac{Q_3}{C_3} = 1,19 \cdot 10^3 \text{ V}$$

$$C_{1,2} = \frac{Q_1 + Q_2}{\Delta V_{1,2}} \Rightarrow \Delta V_{1,2} = \frac{Q_1 + Q_2}{C_{1,2}} = 313 \text{ V}$$

(a) Dall'equiv. tra (a) e (b) scopro che



$$\Delta V_{1,2} = \Delta V_1 \quad \text{e}$$

$$\Delta V_{1,2} = \Delta V_2$$

Calcolo  $Q_1$  e  $Q_2$  avendo il resto:

$$C_1 = \frac{Q_1}{\Delta V_1} \Rightarrow Q_1 = C_1 \Delta V_1 = 110 \text{ nC}$$
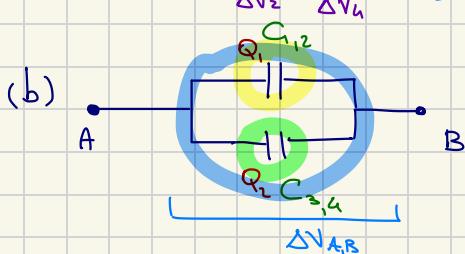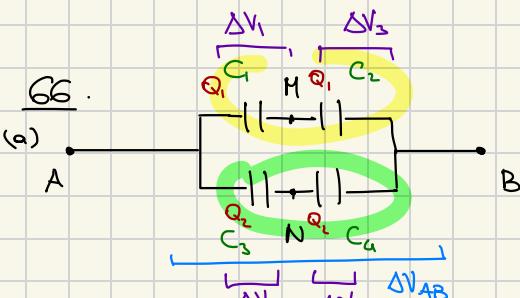
$$Q_2 = C_2 \Delta V_2 = 163 \text{ nC}$$




$$\begin{aligned} C_1 &= 1 \text{ nF} \\ C_2 &= 2 \text{ nF} \\ C_3 &= 3 \text{ nF} \end{aligned} \quad C_4 = ?$$

$$\begin{aligned} \text{Sai che } V_M - V_N &= 0 \\ V_M &= V_N \end{aligned}$$

↳ Ottengo che  $\Delta V_1 = V_M - V_A$   
 è uguale a  $\Delta V_2 = V_N - V_A$   
 $\Delta V_1 = \Delta V_2$

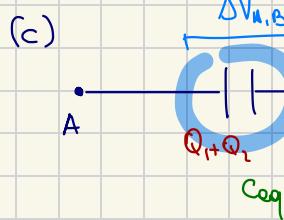Allo stesso modo  $\Delta V_3 = \Delta V_4$



$$C_{eq} = C_{1,2} + C_{3,4}$$

$$(c) C_{eq} = \frac{C_1 C_2}{C_1 + C_2} + \frac{C_3 C_4}{C_3 + C_4}$$

Formule  
capacità

$$(c) C_{eq} = \frac{Q_1 + Q_2}{\Delta V_{eq}}$$

(b)

$$C_{3,4} = \frac{Q_2}{\Delta V_{eq}}$$

$$C_{1,2} = \frac{Q_1}{\Delta V_{eq}}$$

(a)  $\Delta V_1 = \Delta V_2$

;

$$\frac{Q_1}{C_1} = \frac{Q_2}{C_2}$$

inseq. de ci de x2  
problema. IMP!!!