


Settimana: 16

Argomenti:

Materia: Fisica

Classe: 5F

Data: 21/02/2026

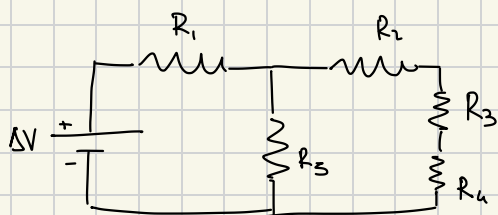

$$R_1 = 80 \, \Omega$$

$$R_2 = R_4 = 10 \, \Omega$$

$$R_3 = 20 \, \Omega$$

$$R_5 = 40 \, \Omega$$


$$\Delta V = 80 \, \text{V}$$

Risolvere il
circuito

Tutte $i = ?$

Tutte $\Delta V = ?$

$R_{eq} = ?$

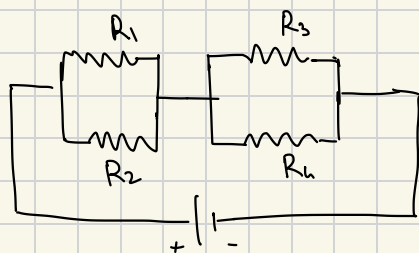

$$\Delta V = 28 \, \text{V}$$

$$R_1 = 300 \, \Omega$$

$$R_2 = 200 \, \Omega$$

$$R_3 = 240 \, \Omega$$

$$R_4 = 480 \, \Omega$$

Tutte $i = ?$

Tutte $\Delta V = ?$

$R_{eq} = ?$